



Q1. (a) Draw a line from each electrical circuit to the correct circuit diagram.
Draw only **four** lines.

electrical circuit

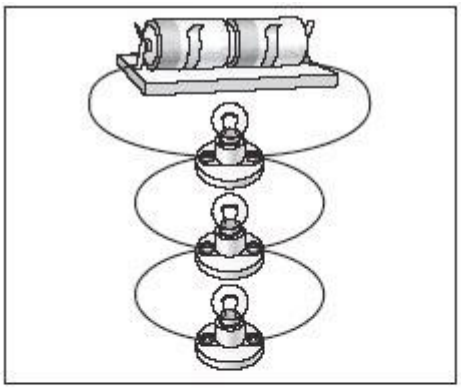


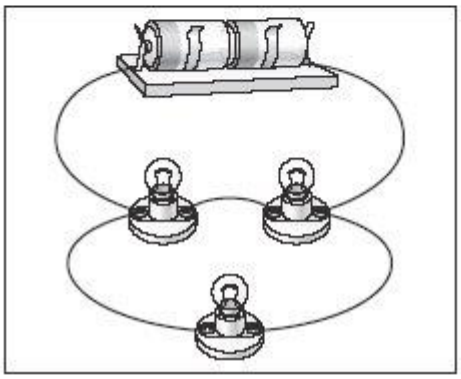


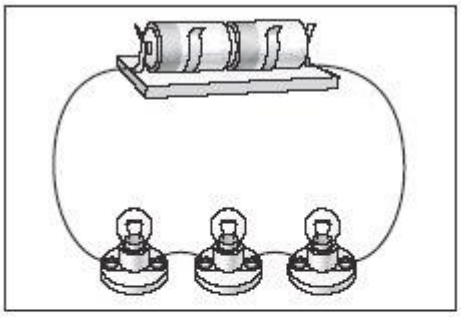


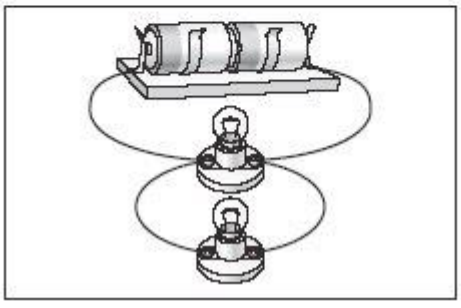


circuit diagram

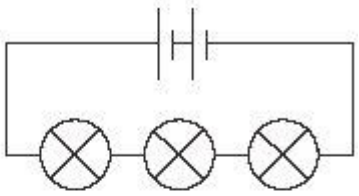

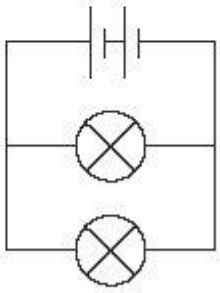

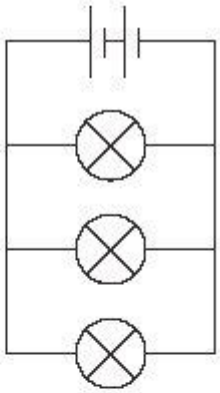


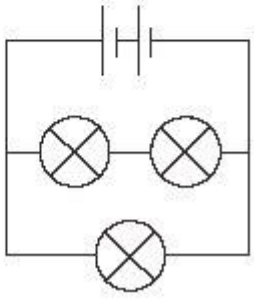


2 marks

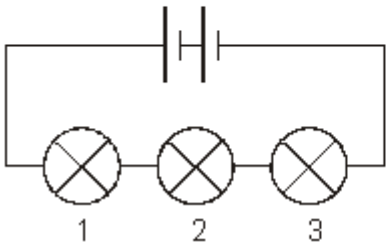(b) In each circuit below, **bulb 1 breaks** and goes off.

Under each circuit diagram below, tick the correct boxes to show if bulb 2 and bulb 3 are **on** or **off**.



circuit A

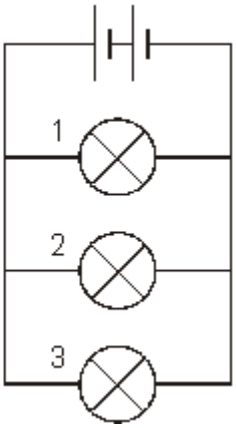

circuit B

	on	off
bulb 1 breaks		?
bulb 2		
bulb 3		

	on	off
bulb 1 breaks		?
bulb 2		
bulb 3		

2 marks

(c) Give the name of the part that provides energy for each circuit.

.....

1 mark

(d) Why is copper used for wires in a circuit?
Tick the correct box.

Copper does **not** stick to a magnet.	☐	Copper is a good conductor of electricity.	☐
Copper is a brown metal.	☐	Copper is a good conductor of heat.	☐


1 mark

maximum 6 marks

Mark schemes

Q1.

(a) •

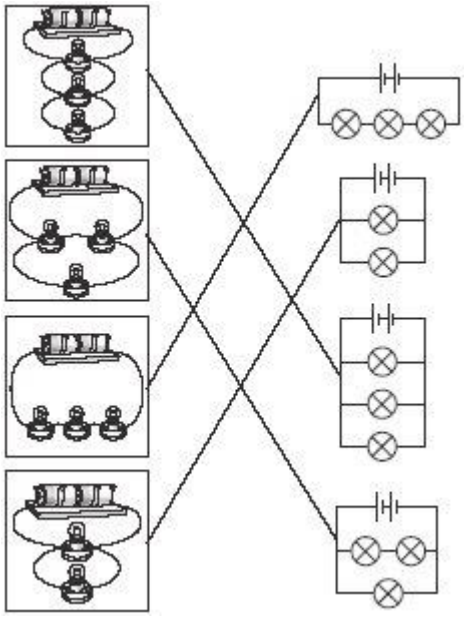

*award two marks for all **four** correct lines*
*award one mark for any **two** or **three** correct lines*
if more than one line is drawn from any box,
do not credit either line

2 (L3)

(b) • off ✓
off ✓

both ticks are required for the mark
if more than one box is ticked in any row, award no mark

1 (L3)

• on ✓
on ✓

both ticks are required for the mark
if more than one box is ticked in any row, award no mark

1 (L4)

(c) • battery

accept 'cell' or 'cells'

1 (L4)

(d) • Copper is a good conductor of electricity. ✓

if more than one box is ticked, award no mark

1 (L3)

[6]